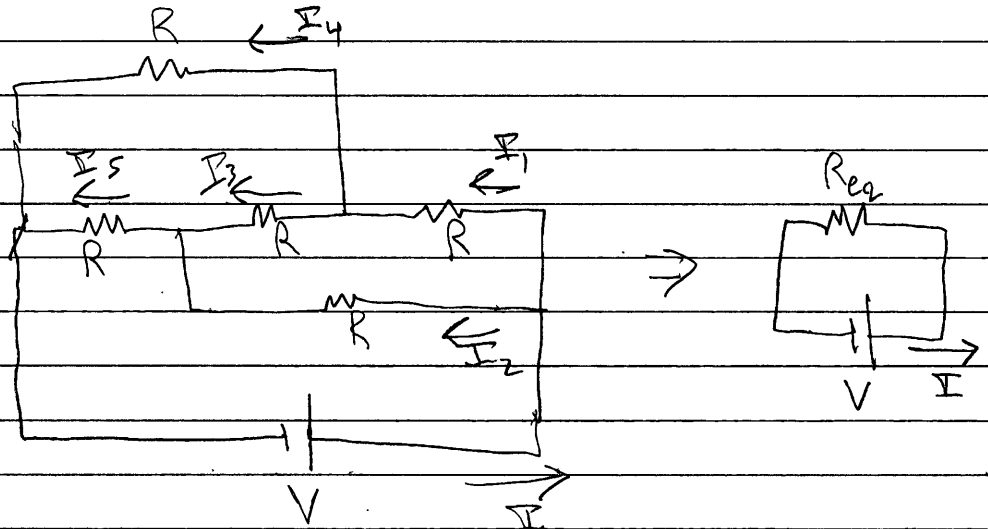


Week 11, Session 2 Solutions

Problem 1.1:



Using Kirchhoff's Laws, we will write down several relations, where we are hoping to solve for I :

Current

$$I = I_1 + I_2 \quad (1)$$

$$I_1 = I_3 + I_4 \quad (2)$$

$$I_3 + I_2 = I_5 \quad (3)$$

$$I = I_4 + I_5 \quad (4)$$

Voltage

$$V = (I_2 + I_5) R \quad (5)$$

$$V = (I_1 + I_4) R \quad (6)$$

$$V = (I_1 + I_3 + I_5) R \quad (7)$$

$$(I_1 + I_3) R = I_2 R \quad (8)$$

$$(I_3 + I_5) R = I_4 R \quad (9)$$

$$V = I \cdot R_{eq} \quad (10)$$

Looking at these equations, we can pick out from adding (5) and (6) that

$$2V = (I_1 + I_2 + I_4 + I_5) R$$


From (1) and (4), this becomes

$$2V = 2IR \Rightarrow I = \frac{V}{R}$$

Then, from (10),

$$V = \frac{V}{R} R_{eq} \Rightarrow R_{eq} = R$$

Problem 1.2:

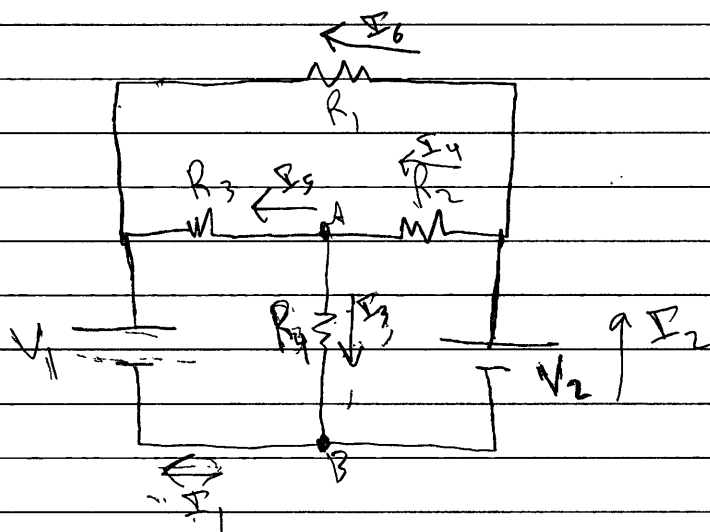

From the voltage rule,

$$V_2 = I_3 R_3 + I_4 R_2 \Rightarrow I_4 = \frac{V_2 - I_3 R_3}{R_2} = \frac{20 - 12}{2} = 4 \text{ A}$$

Then, at node A,

$$I_4 = I_3 + I_5 \Rightarrow I_5 = I_4 - I_3 = 4 - 3 = 1 \text{ A}$$

Over the small loop with V_1 ,

$$V_1 + I_5 R_3 = I_3 R_4 \Rightarrow V_1 = (I_3 - I_5) R_4 = (3 - 1) \cdot 9 = 18 \text{ V}$$

Now, through the outer loop,

$$V_2 - V_1 = I_6 R_1 \Rightarrow I_6 = \frac{V_2 - V_1}{R_1} = \frac{20 - 9}{4} = 11 \text{ A}$$

Now,

$$I_2 = I_4 + I_6 = 15 \text{ A}$$

So

$$I_3 = I_1 + I_2 \Rightarrow I_1 = I_3 - I_2 = -12 \text{ A}$$

This just means the direction of I_1 is opposite what we drew.

(a) $I_3 = 3 \text{ A}$, $I_4 = 4 \text{ A}$, $I_5 = 1 \text{ A}$, $I_6 = 11 \text{ A}$

(b) $V_1 = 18 \text{ V}$

(c) $P_2 = I_2 V_2 = (15)(20) = 300 \text{ W}$
 $P_1 = I_1 V_1 = (-12)(18) = -216 \text{ W}$

Problem 1.3:

(a) $V_1 = Q_0/C_1$, so immediately after the switch is closed,

$$I = V/R = \frac{Q_0}{C_1 R}$$

(b) We will need $V_1 = V_2$, so

$$Q_1/C_1 = Q_2/C_2$$

and

$$\begin{aligned} Q_1 + Q_2 &= Q_0 \Rightarrow Q_0 - Q_2 = Q_2 \frac{C_1}{C_2} \\ &\Rightarrow Q_2 = Q_0 / (1 + C_1/C_2) \\ &\Rightarrow Q_1 = Q_0 / (1 + C_2/C_1) \end{aligned}$$

(c) Our loop has the total voltage drop

$$\begin{aligned} Q_1(t)/C_1 + \frac{dQ_1(t)}{dt} R &= Q_2(t)/C_2 \\ \Rightarrow -\frac{dQ_2}{dt} R &= \frac{Q_2}{C_2} - \frac{Q_0 - Q_2}{C_1} \\ \Rightarrow -C_2 R \frac{dQ_2}{dt} &= Q_2 (1 + C_2/C_1) - C_2 Q_0/C_1 \\ \Rightarrow -\frac{dQ_2}{dt} + Q_2 \frac{1}{RC_2} (1 + \frac{C_2}{C_1}) &= -\frac{Q_0}{C_1 R} \end{aligned}$$

This is of the form

$$\dot{y} + ay = b$$

which is rewritten to have the solution

$$\frac{d}{dt}(y e^{at}) = b e^{at} \Rightarrow y e^{at} = \frac{b}{a} e^{at} + C \Rightarrow y = \frac{b}{a} + C e^{-at}$$

Therefore,

$$Q_2(t) = \frac{C_2}{C_1 + C_2} Q_0 + C e^{-\frac{C_1 + C_2}{R C_1 C_2} t}$$


At $t=0$, $Q_2=0$, so $C = -\frac{C_2}{C_1 + C_2} Q_0$

$$Q_2(t) = \frac{C_2}{C_1 + C_2} Q_0 (1 - e^{-\frac{C_1 + C_2}{R C_1 C_2} t})$$

(d) If C_1 changes by a factor of ϵ :

$$Q_2(t) = \frac{\epsilon C_2}{\epsilon C_1 + C_2} Q_0 (1 - e^{-\frac{C_1 + \epsilon C_1}{R \epsilon C_1 C_2} t})$$

Problem 1.4:

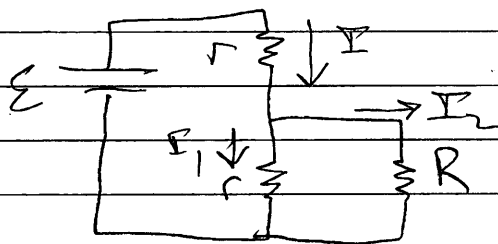

We have

$$I = I_1 + I_2 \quad (1)$$

$$\mathcal{E} = (I + I_1)r \quad (2)$$

$$I_1 r = I_2 R \quad (3)$$

From (1) and (3),

$$I = I_1 \left(1 + \frac{R}{r}\right) \Rightarrow I_1 = I \frac{r}{r+R}$$

Then, from (3),

$$I_2 = I_1 \frac{r}{R} = I \frac{r}{r+R}$$

So the power through this resistor is

$$\begin{aligned} P &= I_2^2 R \\ &= I^2 \frac{R r^2}{(r+R)^2} \end{aligned}$$

Now, if we want this power to stay constant even if R varies slightly, we write

$$\begin{aligned} P &= I^2 r^2 \frac{R + \Delta R}{(r + R + \Delta R)^2} \\ &\approx I^2 r^2 \left[\frac{R + \Delta R}{(r+R)^2} \left(1 + \frac{\Delta R}{r+R}\right)^{-2} \right] \\ &= I^2 \frac{r^2 R}{(r+R)^2} \left[\left(1 + \frac{\Delta R}{R}\right) \left(1 + \frac{\Delta R}{r+R}\right)^{-2} \right] \\ &\approx P_0 \left[\left(1 + \frac{\Delta R}{R}\right) \left(1 - \frac{2\Delta R}{r+R}\right) \right] \\ &= P_0 \left(1 + \Delta R \left(\frac{1}{R} - \frac{2}{r+R} \right) + \Delta R^2 \frac{2}{R(r+R)} \right) \end{aligned}$$

We ignore second order small terms and to have the ΔR coefficient go to zero,

$$\frac{1}{R} = \frac{2}{r+R} \Rightarrow r+R = 2R \Rightarrow r = R$$