

Circuits, Problems


GSI: Caleb Eades

11/1

1 Circuits

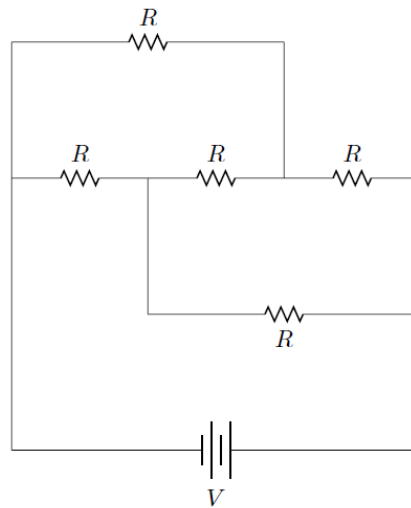1.1 Equivalent Resistance

Find the equivalent resistance of this circuit. Note that it cannot be decomposed into series and parallel.




(Source: Dan and Vetri)

1.2 Kirchhoff Practice

Consider the circuit shown. Suppose the current from A to B is 3 A.

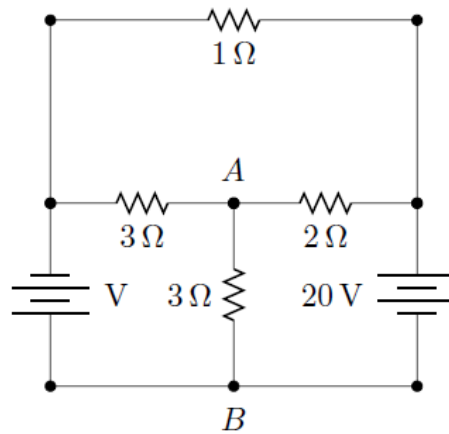- (a) Find the current through each resistor.
- (b) Find the voltage V of the battery on the left.
- (c) Find the power generated by each battery.




(Source: <http://physics.info/kirchhoff/practice.shtml>)

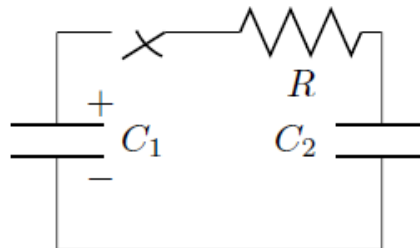1.3 Capacitors in a Circuit

Consider the circuit shown below that contains capacitors C_1 and C_2 and resistor R . Initially the switch is open and the capacitor C_1 has charge Q_0 . The switch is closed at $t = 0$.

- What is the initial current that flows through the resistor right after the switch is closed?
- After a very long time, what are the charges Q_1 and Q_2 on C_1 and C_2 respectively?
- What is the charge $Q_2(t)$ on C_2 as a function of time?
- How will $Q_2(t)$ be modified if a dielectric of constant ϵ is inserted in between the plates of capacitor C_2 ?



(Source: Lanzara Fall 2013 Midterm 2)

1.4

Consider a circuit where a battery leads into a resistor r , which then splits into parallel resistors r and R . If you wanted the power through the resistor R to stay constant even if the resistance R varies slightly, then what value of resistance r should you use for the two other resistors in the circuit?